

# Integrated Circuit Operational Amplifiers

Analog Integrated Circuit Design


A video course under the NPTEL

Nagendra Krishnapura

Department of Electrical Engineering  
Indian Institute of Technology, Madras  
Chennai, 600036, India


National Programme on Technology Enhanced Learning

# Differential pair opamp

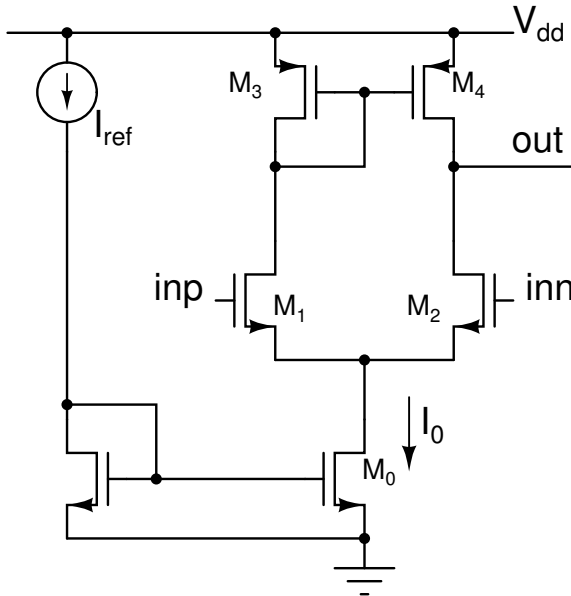

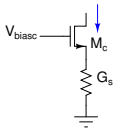
# Cascode output resistance

$$R_{out} = g_{mc}/g_{dsc} G_s + 1/G_s + 1/g_{dsc}$$



$$R_{out} = g_{mc}/g_{dsc} g_{ds1} + 1/g_{dsc} + 1/g_{ds1}$$


(negligible)

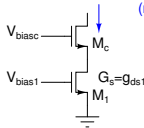

$$R_{out} = g_{mc}/g_{dsc} g_{m1} + 1/g_{dsc} + 1/g_{m1}$$

(negligible)
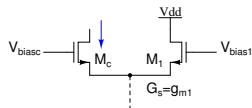
$$R_{out} = 1/g_{dsc} (1 + g_{mc}/g_{m1})$$



differential pair:  $M_C$  degenerated by  $M_1$ 's source impedance ( $g_{m1}$ )



- Output resistance looking into one side of the differential pair is  $2/g_{ds1}$  ( $g_{m1} = g_{mC}$  in the figure)

# Opamp: dc small signal analysis


- Bias values in black
- Incremental values in red
- Impedances in blue

Total quantity = Bias + increment


# Differential pair: Quiescent condition

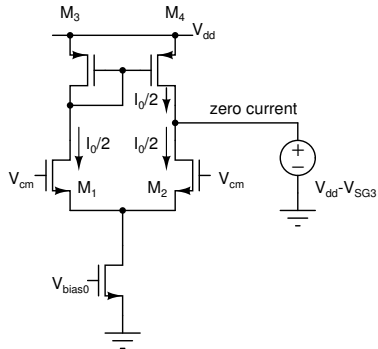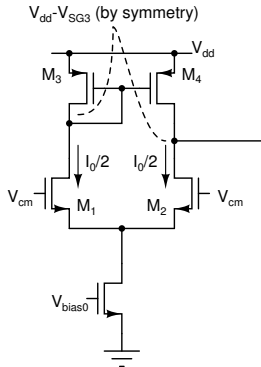


# Differential pair: Transconductance

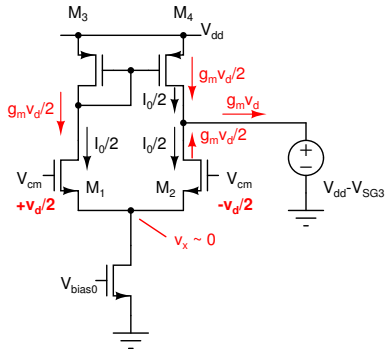

◀ ◻ ▶ ◀ ◻ ▶ ◀ ≡ ▶ ◀ ≡ ▶ ≡

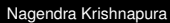

# Differential pair: Noise

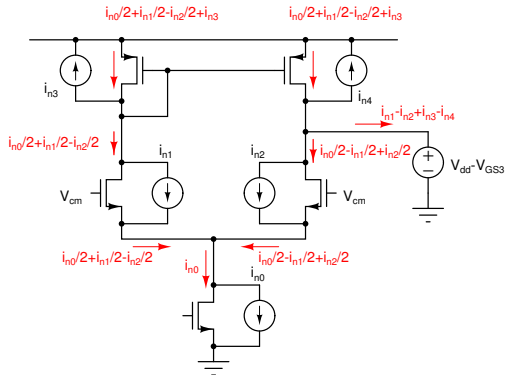


- Carry out small signal linear analysis with one noise source at a time
- Add up the results at the output (current in this case)
- Add up corresponding spectral densities
- Divide by gain squared to get input referred noise




# Differential pair opamp

|                  |  |
|------------------|--|
| $G_m$            | $g_{m1}$   |
| $G_{out}$        | $g_{ds1} + g_{ds3}$  |
| $A_o$            | $g_{m1}/(g_{ds1} + g_{ds3})$   |
| $A_{cm}$         | $g_{ds0}/2g_{m3}$  |
| $C_i$            | $C_{gs1}/2$  |
| $\omega_u$       | $g_{m1}/C_L$   |
| $p_k, z_k$       | $p_2 = -g_{m3}/(C_{db1} + C_{db3} + 2C_{gs3}); z_1 = 2p_2$                           |
| $S_{vi}$         | $16kT/3g_{m1} (1 + g_{m3}/g_{m1})$   |
| $\sigma_{Vos}^2$ | $\sigma_{VT1}^2 + (g_{m3}/g_{m1})^2 \sigma_{VT3}^2$                                  |
| $V_{cm}$         | $\geq V_{T1} + V_{DSAT1} + V_{DSAT0}$<br>$\leq V_{dd} - V_{DSAT3} - V_{T3} + V_{T1}$ |
| $V_{out}$        | $\geq V_{cm} - V_{T1}$<br>$\leq V_{dd} - V_{DSAT3}$                                  |
| SR               | $\pm I_0/C_L$  |
| $I_{supply}$     | $I_0 + I_{ref}$  |

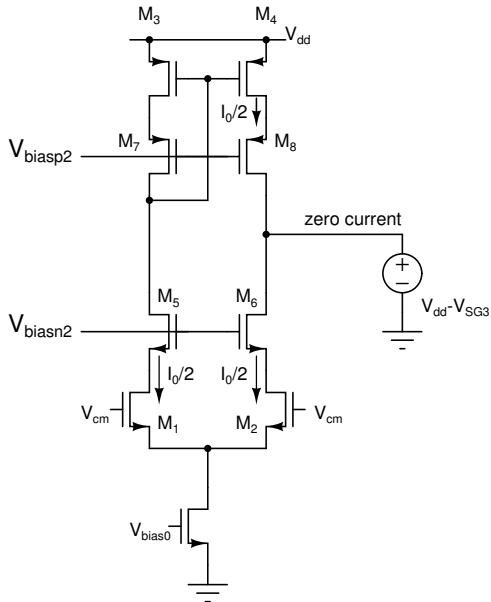
# Telescopic cascode: Quiescent condition




## Telescopic cascode: Transconductance

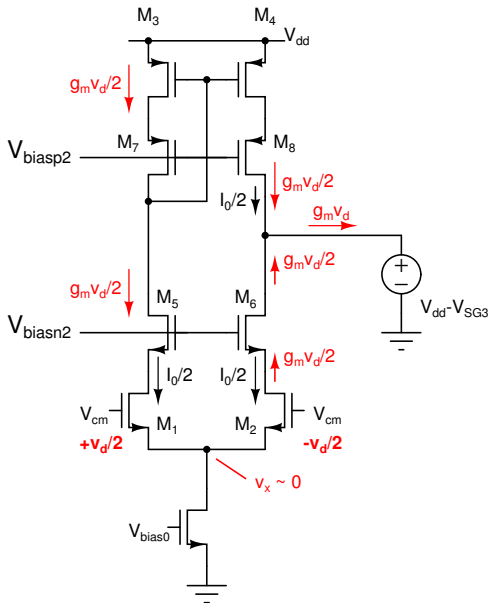

# Telescopic cascode: Output conductance

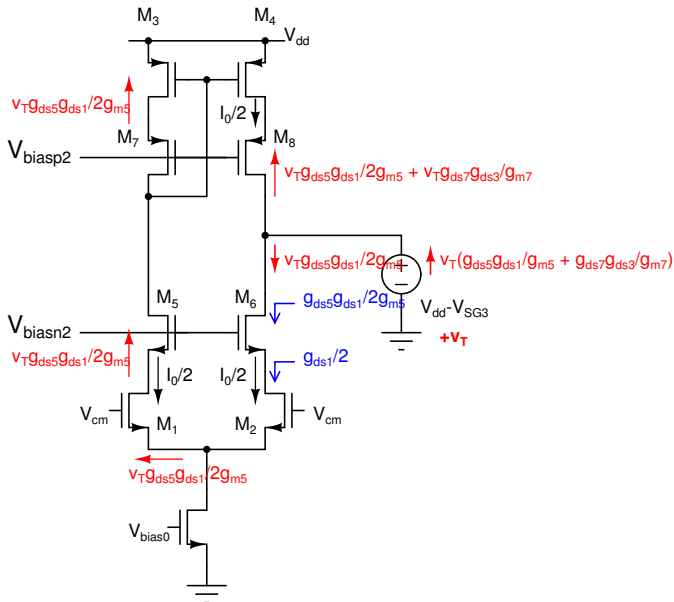


# Telescopic cascode opamp

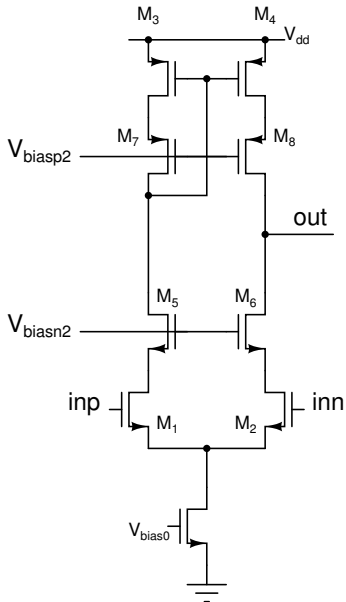


# Telescopic cascode opamp

|                  |  |
|------------------|--|
| $G_m$            | $g_{m1}$   |
| $G_{out}$        | $g_{ds1}g_{ds5}/g_{m5} + g_{ds3}g_{ds7}/g_{m7}$  |
| $A_o$            | $g_{m1}/(g_{ds1}g_{ds5}/g_{m5} + g_{ds3}g_{ds7}/g_{m7})$   |
| $A_{cm}$         | $g_{ds0}/2g_{m3}$  |
| $C_i$            | $C_{gs1}/2$  |
| $\omega_u$       | $g_{m1}/C_L$   |
| $p_k, z_k$       | $p_2 = -g_{m3}/(C_{db1} + C_{db3} + 2C_{gs3})$<br>$p_3 = -g_{m5}/C_{p5}$<br>$p_4 = -g_{m7}/C_{p7}$<br>$p_{2,4}$ appear for one half and cause mirror zeros |
| $S_{vi}$         | $16kT/3g_{m1} (1 + g_{m3}/g_{m1})$   |
| $\sigma_{Vos}^2$ | $\sigma_{VT1}^2 + (g_{m3}/g_{m1})^2 \sigma_{VT3}^2$  |
| $V_{out}$        | $\geq V_{biasn1} - V_{T5}$<br>$\leq V_{biasp1} + V_{T7}$   |
| SR               | $\pm I_0/C_L$  |
| $I_{supply}$     | $I_0 + I_{ref}$  |

# Folded cascode: Quiescent condition

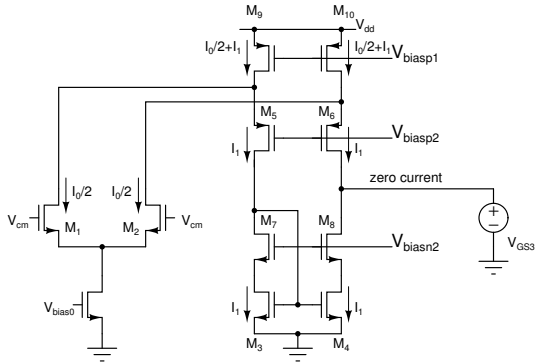


# Folded cascode: Transconductance

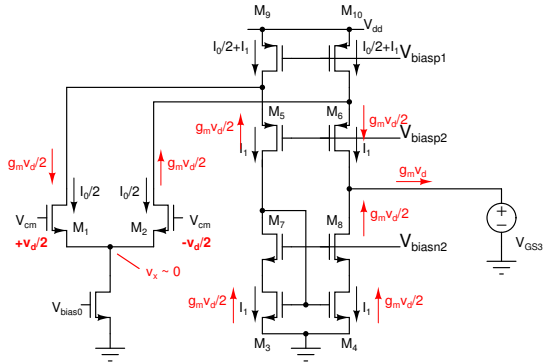




# Folded cascode: Output conductance

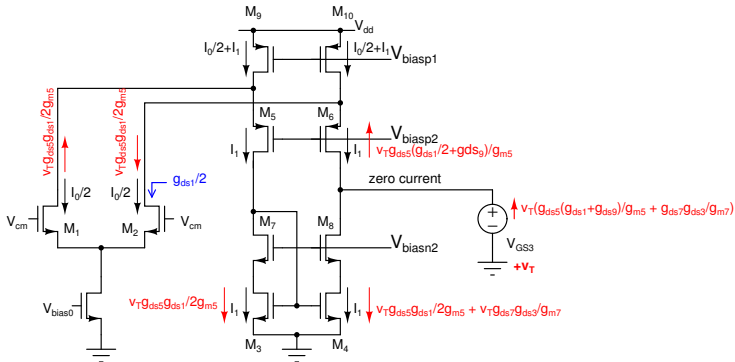

# Folded cascode opamp

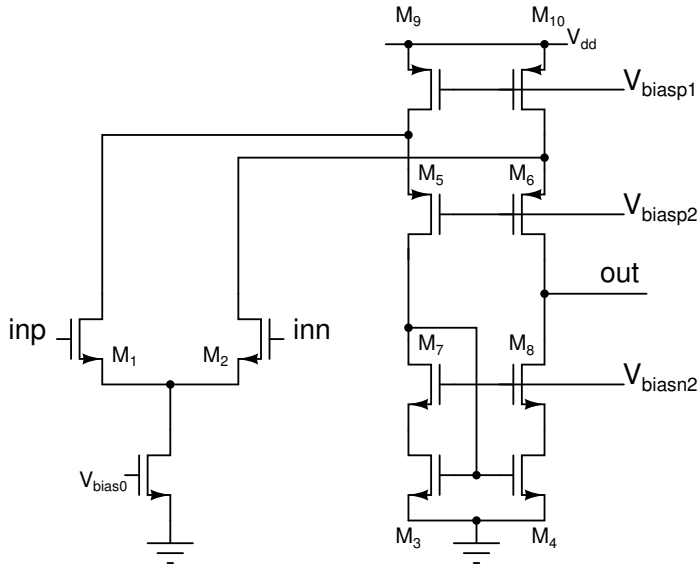


# Folded cascode opamp

|                  |  |
|------------------|--|
| $G_m$            | $g_{m1}$   |
| $G_{out}$        | $(g_{ds1} + g_{ds9})g_{ds5}/g_{m5} + g_{ds3}g_{ds7}/g_{m7}$  |
| $A_o$            | $g_{m1}/((g_{ds1} + g_{ds9})g_{ds5}/g_{m5} + g_{ds3}g_{ds7}/g_{m7})$   |
| $A_{cm}$         | $g_{ds0}/2g_{m3}$  |
| $C_i$            | $C_{gs1}/2$  |
| $\omega_u$       | $g_{m1}/C_L$   |
| $p_k, z_k$       | $p_2 = -g_{m3}/(C_{db1} + C_{db3} + 2C_{gs3})$<br>$p_3 = -g_{m5}/C_{p5}$<br>$p_4 = -g_{m7}/C_{p7}$<br>$p_{2,4}$ appear for one half and cause mirror zeros |
| $S_{vi}$         | $16kT/3g_{m1}(1 + g_{m3}/g_{m1} + g_{m9}/g_{m1})$  |
| $\sigma_{Vos}^2$ | $\sigma_{VT1}^2 + (g_{m3}/g_{m1})^2\sigma_{VT3}^2 + (g_{m9}/g_{m1})^2\sigma_{VT9}^2$   |
| $V_{out}$        | $\geq V_{biasn1} - V_{T5}$<br>$\leq V_{biasp1} + V_{T7}$   |
| SR               | $\pm \min\{I_0, I_1\}/C_L$   |
| $I_{supply}$     | $I_0 + I_1 + I_{ref}$  |


# Body effect

- All nMOS bulk terminals to ground
- All pMOS bulk terminals to  $V_{dd}$
- $A_{cm}$  has an additional factor  $g_{m1}/(g_{m1} + g_{mb1})$
- $g_{m5} + g_{mb5}$  instead of  $g_{m5}$  in cascode opamp results
- $g_{m7} + g_{mb7}$  instead of  $g_{m7}$  in cascode opamp results

# Two stage opamp

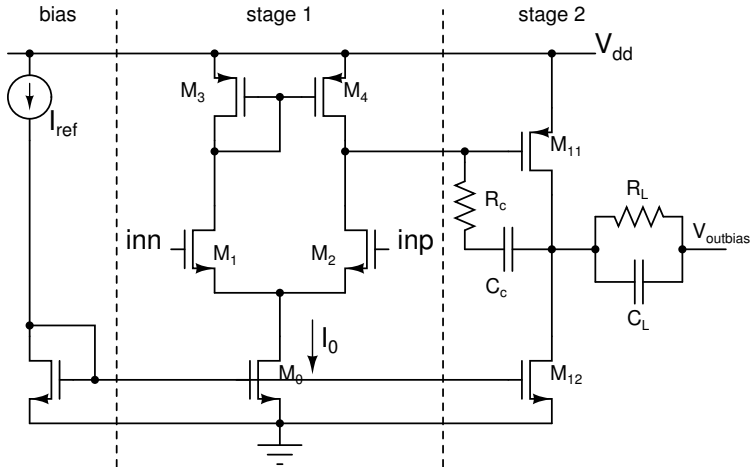

# Two stage opamp

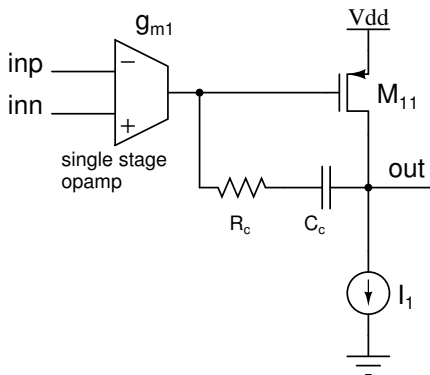

- First stage can be Differential pair, Telescopic cascode, or Folded cascode; Ideal  $g_{m1}$  assumed in the analysis
- Second stage: Common source amplifier
- Frequency response is the product of frequency responses of the first stage  $g_m$  and a common source amplifier driven from a current source

# Common source amplifier: Frequency response

$$\frac{V_o(s)}{V_d(s)} = \left( \frac{g_{m1} g_{m11}}{G_1 G_L} \right) \frac{s C_c (R_c - 1/g_{m11}) + 1}{a_3 s^3 + a_2 s^2 + a_1 s + 1}$$

$$a_3 = \frac{R_c C_1 C_L C_c}{G_1 G_L}$$

$$a_2 = \frac{C_1 C_c + C_c C_L + C_L C_1 + R_c C_c (G_1 C_L + C_1 G_L)}{G_1 G_L}$$

$$a_1 = \frac{C_c (g_{m11} + G_1 + G_L + G_1 G_L R_c) + C_1 G_L + G_1 C_L}{G_1 G_L}$$

- $G_1$ : Total conductive load at the input
- $G_L$ : Total conductive load at the output
- $C_1$ : Total capacitive load at the input
- $C_L$ : Total capacitive load at the output

# Common source amplifier: Poles and zeros

$$\begin{aligned}p_1 &\approx -\frac{G_1}{C_c\left(\frac{g_{m11}}{G_L} + 1 + \frac{G_1}{G_L} + G_1 R_c\right) + C_1\left(1 + \frac{G_1}{G_L}\right)} \\p_2 &\approx -\frac{g_{m11}\frac{C_c}{C_1+C_c} + G_L + G_1\frac{C_c+C_L}{C_1+C_c} + G_1 G_L R_c\frac{C_c}{C_1+C_c}}{\frac{C_1 C_c}{C_1+C_c} + C_L + \frac{R_c C_c (G_1 C_L + G_L C_1)}{C_c+C_L}} \\p_3 &\approx -\left(\frac{1}{R_c}\left(\frac{1}{C_L} + \frac{1}{C_c} + \frac{1}{C_1}\right) + \frac{G_1}{C_1} + \frac{G_L}{C_L}\right) \\z_1 &= \frac{1}{(1/g_{m11} - R_c)C_c}\end{aligned}$$

Unity gain frequency

$$\omega_u \approx \frac{g_{m1}}{C_c\left(1 + \frac{G_L}{g_{m11}} + \frac{G_1}{g_{m11}} + \frac{G_1 G_L R_c}{g_{m11}}\right) + C_1\left(\frac{G_L}{g_{m11}} + \frac{G_1}{g_{m11}}\right)}$$



# Common source amplifier: Frequency response

- Pole splitting using compensation capacitor  $C_c$ 
  - $p_1$  moves to a lower frequency
  - $p_2$  moves to a higher frequency (For large  $C_c$ ,  $p_2 = g_{m11}/C_L$ )
- Zero cancelling resistor  $R_c$  moves  $z_1$  towards the left half  $s$  plane and results in a third pole  $p_3$ 
  - $z_1$  can be moved to  $\infty$  with  $R_c = 1/g_{m11}$
  - $z_1$  can be moved to cancel  $p_2$  with  $R_c > 1/g_{m11}$  (needs to be verified against process variations)
  - Third pole  $p_3$  at a high frequency
- Poles and zeros from the first stage will appear in the frequency response— $Y_{m1}(s)$  instead of  $g_{m1}$  in  $V_o/V_i$  above
  - Mirror pole and zero
  - Poles due to cascode amplifiers

# Compensation cap sizing

$$p_2 \approx -\frac{g_{m11} \frac{C_c}{C_1 + C_c}}{\frac{C_1 C_c}{C_1 + C_c} + C_L}$$

$$\omega_u \approx \frac{g_{m1}}{C_c}$$

Phase margin (Ignoring  $p_3, z_1, \dots$ )

$$\phi_M = \tan^{-1} \frac{|p_2|}{\omega_u}$$

$$\frac{|p_2|}{\omega_u} = \tan \phi_M$$

$$\frac{g_{m11}}{g_{m1}} \left( \frac{C_c}{C_L} \right)^2 = \frac{C_c}{C_L} \left( 1 + \frac{C_1}{C_L} \right) \tan \phi_M + \frac{C_1}{C_L} \tan \phi_M$$

- For a given  $\phi_M$ , solve the quadratic to obtain  $C_c/C_L$
- If  $C_1$  is very small,  $p_2 \approx -g_{m2}/C_L$ ; further simplifies calculations


# Two stage opamp

|                  |  |
|------------------|--|
| $A_o$            | $g_{m1}g_{m11}/(g_{ds1} + g_{ds3})(g_{ds11} + g_{ds12})$                             |
| $A_{cm}$         | $g_{ds0}g_{m11}/2g_{m3}(g_{ds11} + g_{ds12})$  |
| $C_i$            | $C_{gs1}/2$  |
| $\omega_u$       | $g_{m1}/C_c$   |
| $p_k, z_k$       | See previous pages   |
| $S_{vi}$         | $\approx 16kT/3g_{m1}(1 + g_{m3}/g_{m1})$  |
| $\sigma_{Vos}^2$ | $\approx \sigma_{VT1}^2 + (g_{m3}/g_{m1})^2\sigma_{VT3}^2$                           |
| $V_{cm}$         | $\geq V_{T1} + V_{DSAT1} + V_{DSAT0}$<br>$\leq V_{dd} - V_{DSAT3} - V_{T3} + V_{T1}$ |
| $V_{out}$        | $\geq V_{DSAT12}$<br>$\leq V_{dd} - V_{DSAT11}$                                      |
| SR+              | $I_0/C_c$  |
| SR-              | $\min\{I_0/C_c, I_1/(C_L + C_c)\}$   |
| $I_{supply}$     | $I_0 + I_1 + I_{ref}$  |

# Opamp comparison


|        | Differential | Telescopic | Folded  | Two   |
|--------|--------------|------------|---------|-------|
|        | pair         | cascode    | cascode | stage |
| Gain   | —            | ++         | +       | ++    |
| Noise  | =            | =          | high    | =     |
| Offset | =            | =          | high    | =     |
| Swing  | —            | —          | +       | ++    |
| Speed  | ++           | +          | —       | +     |

# Differential pair

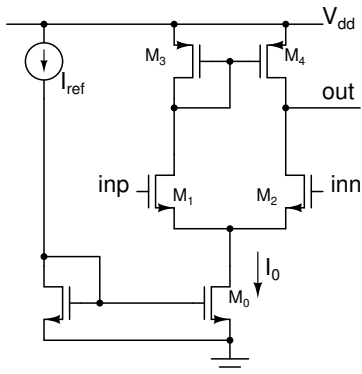


- Low accuracy (low gain) applications
- Voltage follower (capacitive load)
- Voltage follower with source follower (resistive load)
- In bias stabilization loops (effectively two stages in feedback)

# Telescopic cascode

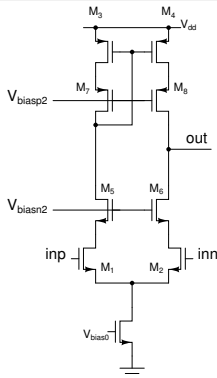


- Low swing circuits
- Switched capacitor circuits
  - Capacitive load
  - Different input and output common mode voltages
- First stage of a two stage opamp
  - Only way to get high gain in fine line processes

# Folded cascode

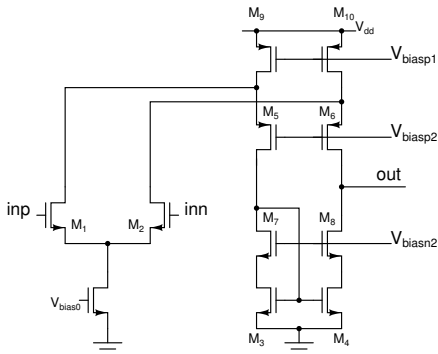

- Higher swing circuits
- Higher noise and offset
- Lower speed than telescopic cascode
  - Low frequency pole at the drain of the input pair
- Switched capacitor circuits (Capacitive load)
- First stage of a two stage class AB opamp

# Two stage opamp

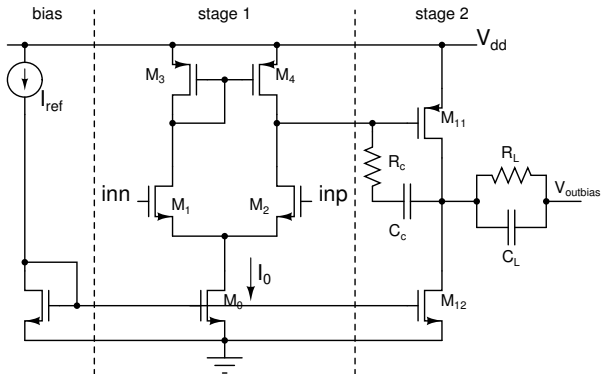



- Highest possible swing
- Resistive loads
- Capacitive loads at high speed
- “Standard” opamp: Miller compensated two stage opamp
- Class AB opamp: Always two (or more) stages



# Opamps: pMOS versus nMOS input stage


- nMOS input stage
  - Higher  $g_m$  for the same current
  - Suitable for large bandwidths
  - Higher flicker noise (usually)
- pMOS input stage
  - Lower  $g_m$  for the same current
  - Lower flicker noise (usually)
  - Suitable for low noise low frequency applications

# Fully differential circuits

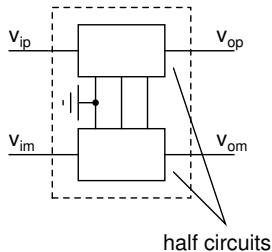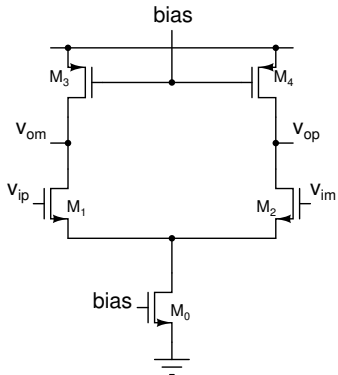

- Two identical half circuits with some common nodes
- Two arms of the differential input applied to each half
- Two arms of the differential output taken from each half


# Differential half circuit

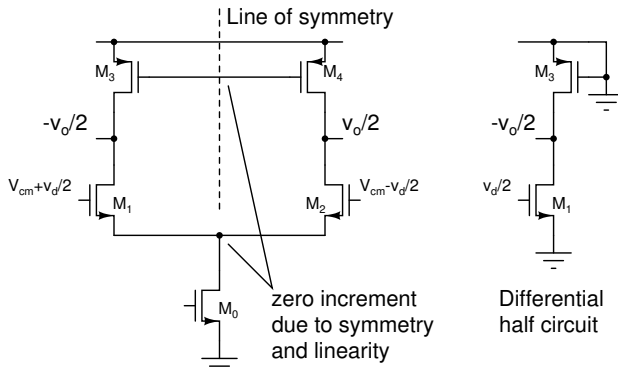

Symmetrical linear (or small signal linear) circuit under fully differential (antisymmetric) excitation

- Nodes along the line of symmetry at 0 V (symmetry, linearity)
- Analyze only the half circuit to find the transfer function


# Common mode half circuit

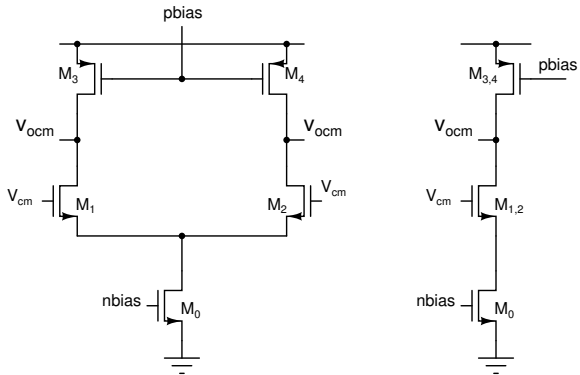

Symmetrical circuit (maybe nonlinear) under common mode (symmetric) excitation


- Nodes in each half at identical voltages (symmetry)
- Fold over the circuit and analyze the half circuit

# Common mode feedback

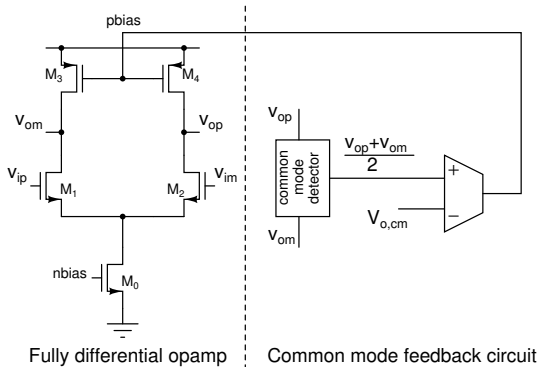



- Common mode feedback circuit for setting the bias
- Detect the output common mode and force it to be  $V_{o,cm}$  via feedback

# Common mode feedback loop

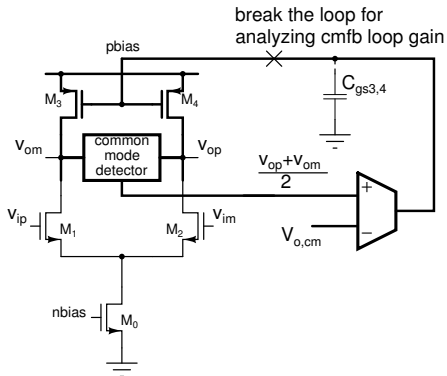

- Common mode feedback loop has to be stable
- Analyze it by breaking the loop and computing the loop gain with appropriate loading at the broken point
- Apply a common mode step/pulse in closed loop and ensure stability

# Fully differential circuits: Noise

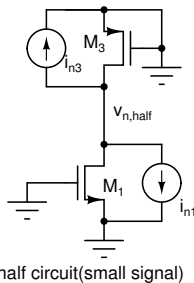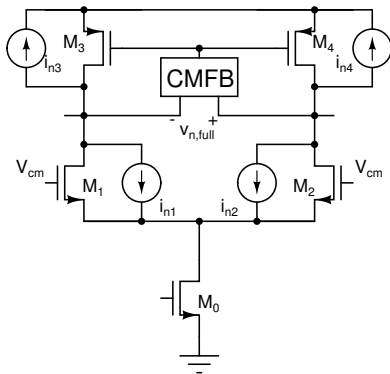


half circuit (small signal)

$$S_{n,full} = 2S_{n,half}$$

- Calculate noise spectral density of the half circuit
- Multiply by  $2\times$



## Fully differential circuits: Offset

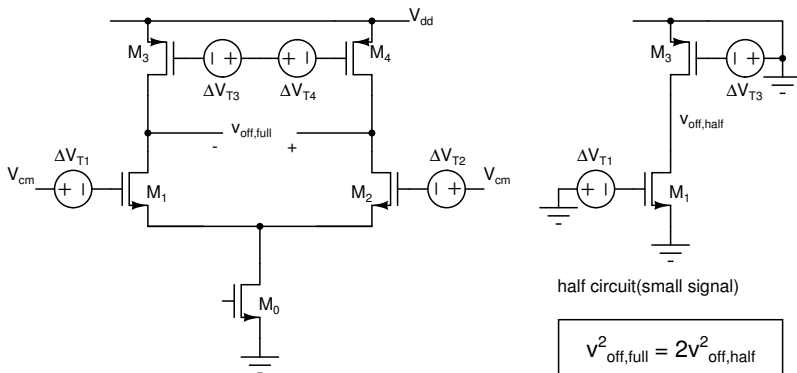

- Calculate mean squared offset of the half circuit
- Multiply by  $2\times$  if mismatch (e.g.  $\Delta V_T$ ) wrt ideal device is used



## Fully differential circuits: Offset

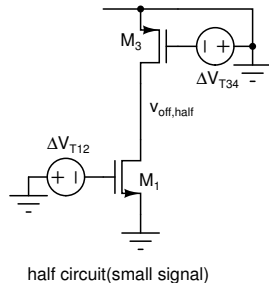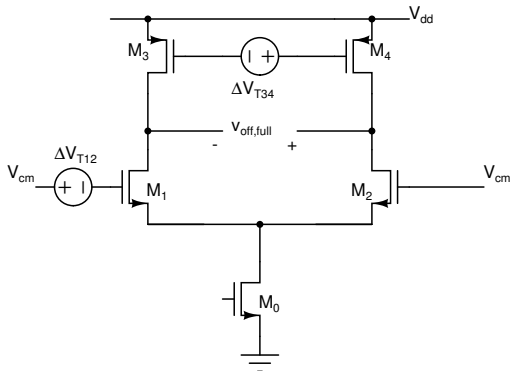

$$v_{\text{off,full}}^2 = v_{\text{off,half}}^2$$

- Calculate mean squared offset of the half circuit
- Multiply by  $1 \times$  if mismatch between two real devices is used