

LECTURE 430 – COMPENSATION OF OP AMPS-II

(READING: Text-Sec. 9.2, 9.3, 9.4)

INTRODUCTION

The objective of this presentation is to continue the ideas of the last lecture on compensation of op amps.

Outline

- Compensation of Op Amps
 - General principles
 - Miller, Nulling Miller
 - Self-compensation
 - Feedforward
- Summary

Conditions for Stability of the Two-Stage Op Amp (Assuming $p_3 \geq GB$)

- Unity-gainbandwidth is given as:

$$GB = A_v(0) \cdot |p_1| = \left(\frac{g_{mI} g_{mII} R_I R_{II}}{g_{mII} R_I R_{II} C_c} \right) = \frac{g_{mI}}{C_c} = \left(\frac{g_{m1} g_{m2} R_1 R_2}{g_{m2} R_1 R_2 C_c} \right) = \frac{g_{m1}}{C_c}$$

- The requirement for 45° phase margin is:

$$\pm 180^\circ - \text{Arg}[AF] = \pm 180^\circ - \tan^{-1} \left(\frac{\omega}{|p_1|} \right) - \tan^{-1} \left(\frac{\omega}{|p_2|} \right) - \tan^{-1} \left(\frac{\omega}{z} \right) = 45^\circ$$

Let $\omega = GB$ and assume that $z \geq 10GB$, therefore we get,

$$\pm 180^\circ - \tan^{-1} \left(\frac{GB}{|p_1|} \right) - \tan^{-1} \left(\frac{GB}{|p_2|} \right) - \tan^{-1} \left(\frac{GB}{z} \right) = 45^\circ$$

$$135^\circ \approx \tan^{-1}(A_v(0)) + \tan^{-1} \left(\frac{GB}{|p_2|} \right) + \tan^{-1}(0.1) = 90^\circ + \tan^{-1} \left(\frac{GB}{|p_2|} \right) + 5.7^\circ$$

$$39.3^\circ \approx \tan^{-1} \left(\frac{GB}{|p_2|} \right) \Rightarrow \frac{GB}{|p_2|} = 0.818 \Rightarrow \boxed{|p_2| \geq 1.22GB}$$

- The requirement for 60° phase margin:

$$\boxed{|p_2| \geq 2.2GB \text{ if } z \geq 10GB}$$


- If 60° phase margin is required, then the following relationships apply:

$$\frac{g_{m6}}{C_c} > \frac{10g_{m1}}{C_c} \Rightarrow \boxed{g_{m6} > 10g_{m1}} \quad \text{and} \quad \frac{g_{m6}}{C_2} > \frac{2.2g_{m1}}{C_c} \Rightarrow \boxed{C_c > 0.22C_2}$$

Controlling the Right-Half Plane Zero

Why is the RHP zero a problem?

 Because it boosts the magnitude but lags the phase - the worst possible combination for stability.



Solution of the problem:

If zeros are caused by two paths to the output, then eliminate one of the paths.

Use of Buffer to Eliminate the Feedforward Path through the Miller Capacitor

Model:

The transfer function is given by the following equation,

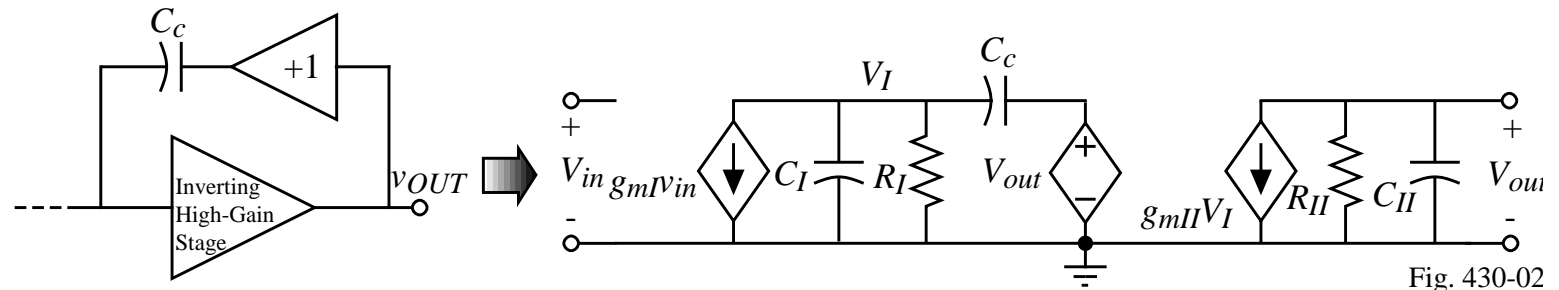


Fig. 430-02

$$\frac{V_o(s)}{V_{in}(s)} = \frac{(g_{mI})(g_{mII})(R_I)(R_{II})}{1 + s[R_IC_I + R_{II}C_{II} + R_IC_c + g_{mII}R_IR_{II}C_c] + s^2[R_IR_{II}C_{II}(C_I + C_c)]}$$

Using the technique as before to approximate p_1 and p_2 results in the following

$$p_1 \cong \frac{-1}{R_IC_I + R_{II}C_{II} + R_IC_c + g_{mII}R_IR_{II}C_c} \cong \frac{-1}{g_{mII}R_IR_{II}C_c}$$

and

$$p_2 \cong \frac{-g_{mII}C_c}{C_{II}(C_I + C_c)}$$

Comments:

Poles are approximately what they were before with the zero removed.


For 45° phase margin, $|p_2|$ must be greater than GB

For 60° phase margin, $|p_2|$ must be greater than $1.73GB$

Use of Buffer with Finite Output Resistance to Eliminate the RHP Zero

Assume that the unity-gain buffer has an output resistance of R_o .

Model:

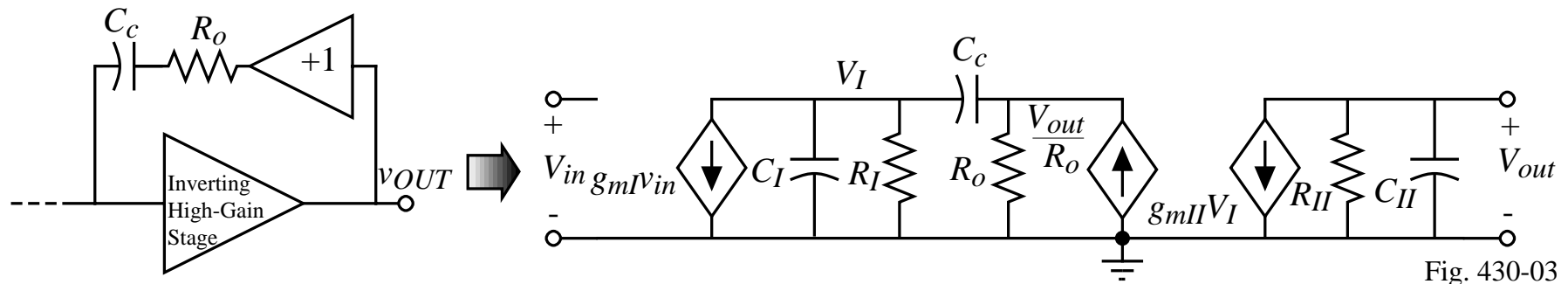

It can be shown that if the output resistance of the buffer amplifier, R_o , is not neglected that another pole occurs at,


$$p_4 \cong \frac{-1}{R_o[C_I C_c / (C_I + C_c)]}$$

and a LHP zero at

$$z_2 \cong \frac{-1}{R_o C_c}$$

Closer examination shows that if a resistor, called a *nulling resistor*, is placed in series with C_c that the RHP zero can be eliminated or moved to the LHP.

 Use of Nulling Resistor to Eliminate the RHP Zero (or turn it into a LHP zero)[†]



Nodal equations:

$$g_{mI}V_{in} + \frac{V_I}{R_I} + sC_IV_I + \left(\frac{sC_c}{1 + sC_cR_z} \right) (V_I - V_{out}) = 0$$

$$g_{mII}V_I + \frac{V_o}{R_{II}} + sC_{II}V_{out} + \left(\frac{sC_c}{1 + sC_cR_z} \right) (V_{out} - V_I) = 0$$

Solution:

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{a\{1 - s[(C_c/g_{mII}) - R_zC_c]\}}{1 + bs + cs^2 + ds^3}$$

where

$$a = g_{mI}g_{mII}R_IR_{II}$$

$$b = (C_{II} + C_c)R_{II} + (C_I + C_c)R_I + g_{mII}R_IR_{II}C_c + R_zC_c$$

$$c = [R_IR_{II}(C_IC_{II} + C_cC_I + C_cC_{II}) + R_zC_c(R_IC_I + R_{II}C_{II})]$$

$$d = R_IR_{II}R_zC_IC_{II}C_c$$

[†] W.J. Parrish, "An Ion Implanted CMOS Amplifier for High Performance Active Filters", Ph.D. Dissertation, 1976, Univ. of CA., Santa Barbara.

Use of Nulling Resistor to Eliminate the RHP - Continued

If R_z is assumed to be less than R_I or R_{II} and the poles widely spaced, then the roots of the above transfer function can be approximated as

$$p_1 \cong \frac{-1}{(1 + g_{mII}R_{II})R_IC_c} \cong \frac{-1}{g_{mII}R_{II}R_IC_c}$$

$$p_2 \cong \frac{-g_{mII}C_c}{C_IC_{II} + C_cC_I + C_cC_{II}} \cong \frac{-g_{mII}}{C_{II}}$$

$$p_4 = \frac{-1}{R_zC_I}$$

and

$$z_1 = \frac{1}{C_c(1/g_{mII} - R_z)}$$

Note that the zero can be placed anywhere on the real axis.

Conceptual Illustration of the Nulling Resistor Approach

 


Fig. Fig. 430-05

The output voltage, V_{out} , can be written as

$$V_{out} = \frac{-g_{m6}R_{II}\left(R_z + \frac{1}{sC_c}\right)}{R_{II} + R_z + \frac{1}{sC_c}} V' + \frac{R_{II}}{R_{II} + R_z + \frac{1}{sC_c}} V'' = \frac{-R_{II}\left[g_{m6}R_z + \frac{g_{m6}}{sC_c} - 1\right]}{R_{II} + R_z + \frac{1}{sC_c}} V$$

when $V = V' = V''$.

Setting the numerator equal to zero and assuming $g_{m6} = g_{mII}$ gives,

$$z_1 = \frac{1}{C_c(1/g_{mII} - R_z)}$$

A Design Procedure that Allows the RHP Zero to Cancel the Output Pole, p_2

We desire that $z_1 = p_2$ in terms of the previous notation.

Therefore,

$$\frac{1}{C_c(1/g_{mII} - R_z)} = \frac{-g_{mII}}{C_{II}}$$

The value of R_z can be found as

$$R_z = \left(\frac{C_c + C_{II}}{C_c} \right) (1/g_{mII})$$

With p_2 canceled, the remaining roots are p_1 and p_4 (the pole due to R_z). For unity-gain stability, all that is required is that

$$|p_4| > A_v(0)|p_1| = \frac{A_v(0)}{g_{mII}R_{II}R_IC_c} = \frac{g_{mI}}{C_c}$$

and


$$(1/R_z C_I) > (g_{mI}/C_c) = GB$$

Substituting R_z into the above inequality and assuming $C_{II} \gg C_c$ results in

$$C_c > \sqrt{\frac{g_{mI}}{g_{mII}}} C_I C_{II}$$

This procedure gives excellent stability for a fixed value of C_{II} ($\approx C_L$).

 Unfortunately, as C_L changes, p_2 changes and the zero must be readjusted to cancel p_2 .



Increasing the Magnitude of the Output Pole[†]

The magnitude of the output pole, p_2 , can be increased by introducing gain in the Miller capacitor feedback path. For example,

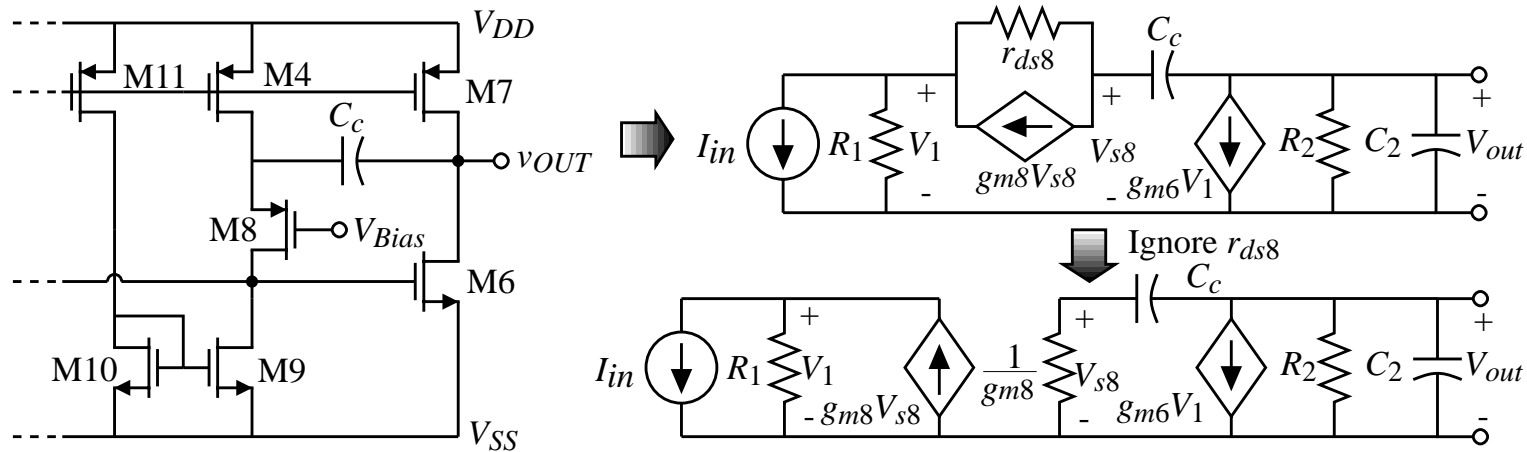


Fig. 430-07

The resistors R_1 and R_2 are defined as

$$R_1 = \frac{1}{g_{ds2} + g_{ds4} + g_{ds9}} \quad \text{and} \quad R_2 = \frac{1}{g_{ds6} + g_{ds7}}$$

where transistors M2 and M4 are the output transistors of the first stage.

Nodal equations:

$$I_{in} = G_1 V_1 - g_{m8} V_{s8} = G_1 V_1 - \left(\frac{g_{m8} s C_c}{g_{m8} + s C_c} \right) V_{out} \quad \text{and} \quad 0 = g_{m6} V_1 + \left[G_2 + s C_2 + \frac{g_{m8} s C_c}{g_{m8} + s C_c} \right] V_{out}$$

[†] B.K. Ahuja, "An Improved Frequency Compensation Technique for CMOS Operational Amplifiers," *IEEE J. of Solid-State Circuits*, Vol. SC-18, No. 6 (Dec. 1983) pp. 629-633.

Increasing the Magnitude of the Output Pole - Continued

Solving for the transfer function V_{out}/I_{in} gives,

$$\frac{V_{out}}{I_{in}} = \left(\frac{-g_{m6}}{G_1 G_2} \right) \left[\frac{\left(1 + \frac{sC_c}{g_{m8}} \right)}{1 + s \left[\frac{C_c}{g_{m8}} + \frac{C_2}{G_2} + \frac{C_c}{G_2} + \frac{g_{m6}C_c}{G_1 G_2} \right] + s^2 \left(\frac{C_c C_2}{g_{m8} G_2} \right)} \right]$$

Using the approximate method of solving for the roots of the denominator gives

$$p_1 = \frac{-1}{\frac{C_c}{g_{m8}} + \frac{C_c}{G_2} + \frac{C_2}{G_2} + \frac{g_{m6}C_c}{G_1 G_2}} \approx \frac{-6}{g_{m6}r_{ds}^2 C_c}$$

and

$$p_2 \approx \frac{-\frac{g_{m6}r_{ds}^2 C_c}{6}}{\frac{C_c C_2}{g_{m8} G_2}} = \frac{g_{m8}r_{ds}^2 G_2}{6} \left(\frac{g_{m6}}{C_2} \right) = \left(\frac{g_{m8}r_{ds}}{3} \right) |p_2'|$$

where all the various channel resistance have been assumed to equal r_{ds} and p_2' is the output pole for normal Miller compensation.

Result:

Dominant pole is approximately the same and the output pole is increased by $\approx g_m r_{ds}$.

Concept Behind the Increasing of the Magnitude of the Output Pole

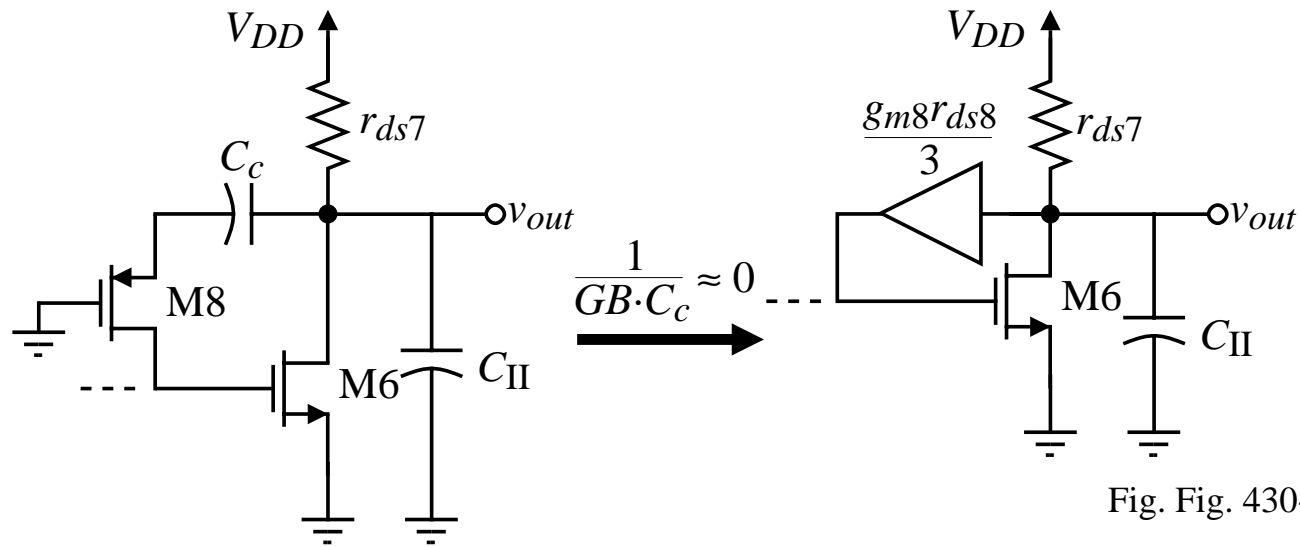


Fig. Fig. 430-08

$$R_{out} = r_{ds7} \parallel \left(\frac{3}{g_{m6}g_{m8}r_{ds8}} \right) \approx \frac{3}{g_{m6}g_{m8}r_{ds8}}$$

Therefore, the output pole is approximately,

$$|p_2| \approx \frac{g_{m6}g_{m8}r_{ds8}}{3C_{II}}$$

FEEDFORWARD COMPENSATION

Use two parallel paths to achieve a LHP zero for lead compensation purposes.

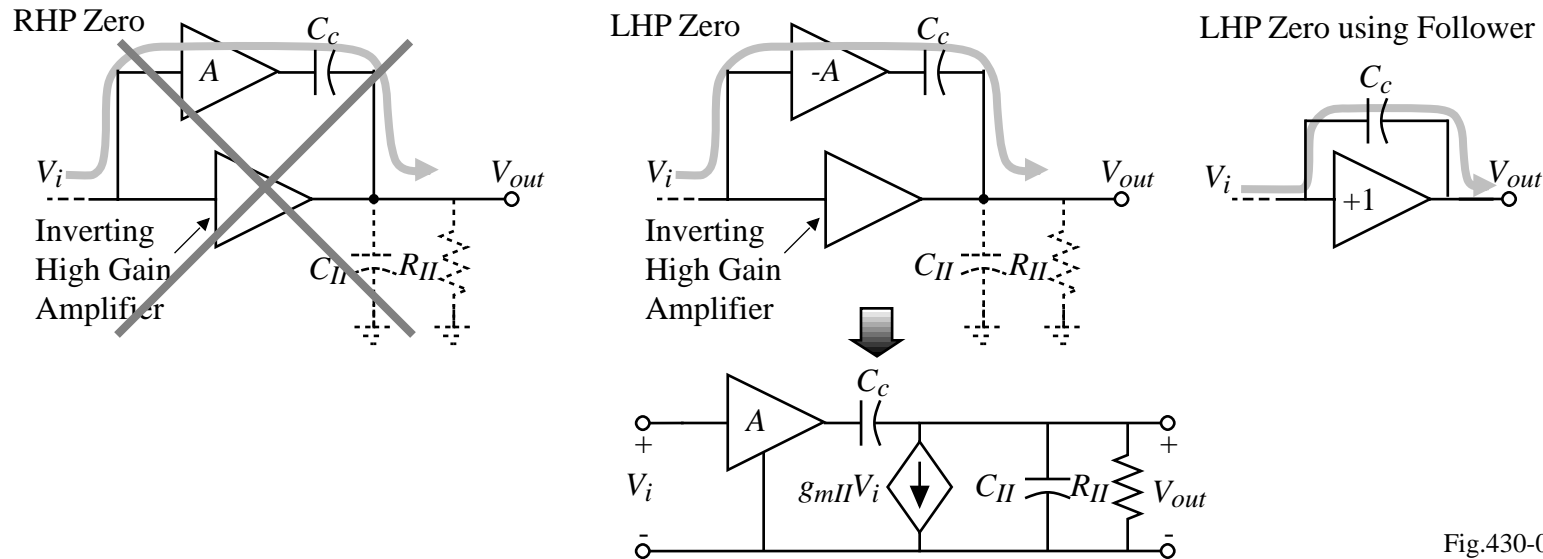


Fig.430-09

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{AC_c}{C_c + C_{II}} \left(\frac{s + g_{mII}/AC_c}{s + 1/[R_{II}(C_c + C_{II})]} \right)$$


To use the LHP zero for compensation, a compromise must be observed.

- Placing the zero below GB will lead to boosting of the loop gain that could deteriorate the phase margin.
- Placing the zero above GB will have less influence on the leading phase caused by the zero.

Note that a source follower is a good candidate for the use of feedforward compensation.

SELF-COMPENSATED OP AMPS

 Self compensation occurs when the load capacitor is the compensation capacitor (can never be unstable for resistive feedback)



Voltage gain:

$$\frac{v_{out}}{v_{in}} = A_v(0) = G_m R_{out}$$

Dominant pole:

$$p_1 = \frac{-1}{R_{out} C_L}$$

Unity-gainbandwidth:

$$GB = A_v(0) \cdot |p_1| = \frac{G_m}{C_L}$$

Stability:

Large load capacitors simply reduce GB but the phase is still 90° at GB .

SUMMARY

Compensation

- Designed so that the op amp with unity gain feedback (buffer) is stable
- Types
 - Miller
 - Miller with nulling resistors
 - Self Compensating
 - Feedforward